Design a binary to Gray code converter and explain its working and applications.

TEAM MEMBERS:

- Anjana Varma - 2620030395
- Divija Laxmi - 2620030338
- Ganesh Goud - 2620030371
- Bindu Sri - 2620030264

Problem Statement

- Binary code is widely used in digital systems to represent numbers and data.
- When binary numbers change from one value to the next, multiple bits may change simultaneously.
- This can cause temporary incorrect readings due to differences in signal timing.
- Gray code reduces this problem because only one bit changes between consecutive values.
- Therefore, this project aims to design a Binary to Gray Code Converter using combinational logic circuits.

Introduction

- Binary code represents numbers using only 0 and 1.
- Gray code is a binary coding system in which consecutive numbers differ by only one bit.
- It helps reduce errors caused by multiple bits changing simultaneously.
- It is used in digital electronics and position-encoding systems.
- A Binary to Gray Code Converter converts a binary input into its equivalent Gray code output.

Example:

Decimal	Binary	Gray Code
0	000	000
1	001	001
2	010	011
3	011	010

Background Study

Binary Code:

- Uses 0 and 1 to represent numbers.
- Multiple bits may change when moving between consecutive values.
- Example: 0111 → 1000 changes all four bits.

Gray Code:

- Only one bit changes between consecutive values.
- Reduces errors caused by simultaneous bit transitions.
- Example: 0100 → 1100 changes only one bit.


Conversion Method:

- Gray code is generated by keeping the MSB unchanged and applying XOR operations to adjacent binary bits.

Design/Methodology

- For a 4-bit binary input B3,B2,B1,B0 the output equations are:
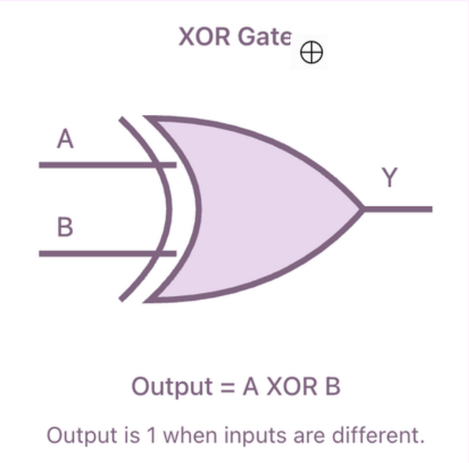
$$G3 = B3$$
$$G2 = B3 \oplus B2$$
$$G1 = B2 \oplus B1$$
$$G0 = B1 \oplus B0$$



Explanation:

- The most significant bit is directly connected to the output.
- The remaining outputs are generated using XOR gates.
- The circuit requires 3 XOR gates and 1 direct connection.

Circuit Diagram

Circuit Diagram of Binary to Gray Code Converter:


The 4-bit binary-to-Gray code converter is designed using XOR gates and a direct connection. The circuit takes four binary inputs and produces four Gray code outputs.

Circuit Connections:

Binary input(s)	Operation	Gray output
B3	Direct connection	G3
B3, B2	XOR gate	G2
B2, B1	XOR gate	G1
B1, B0	XOR gate	G0

- Four input pins on the left: B3, B2, B1, B0.
- Three XOR gates in the middle.
- Four output pins on the right: G3, G2, G1, G0.
- Connect the inputs according to the table.

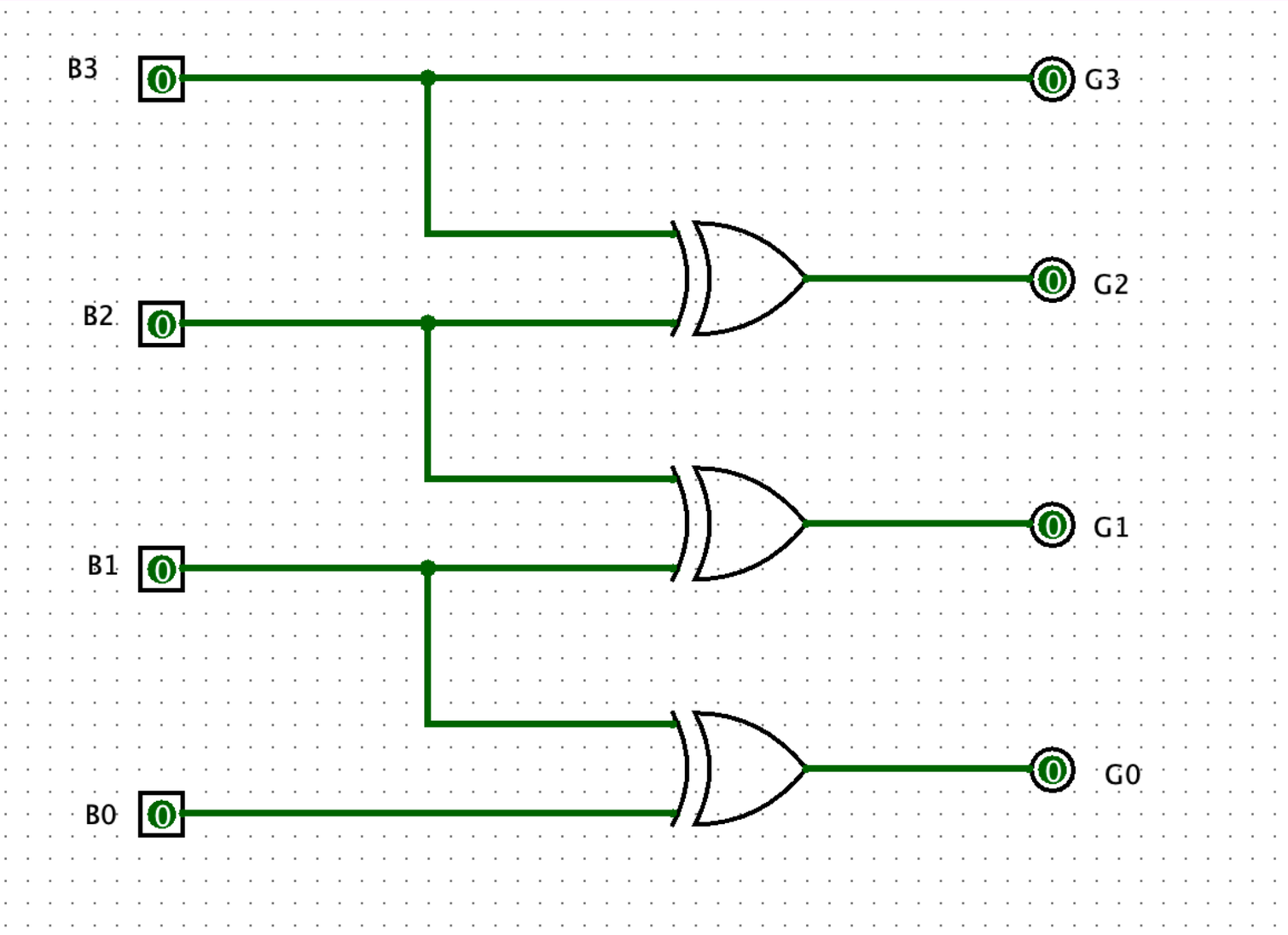Circuit Diagram – Logisim Implementation.



TruthTable

Truth Table and Working Principle:

The truth table shows the conversion of all 16 possible 4-bit binary inputs into their corresponding Gray code outputs. The most significant bit remains. unchanged, and each remaining Gray bit is obtained by XOR-ing two adjacent binary bits.

For binary input 1010:

- **G3 = 1**
- **G2 = 1 XOR 0 = 1**
- **G1 = 0 XOR 1 = 1**
- **G0 = 1 XOR 0 = 1**

Therefore, Binary 1010 → Gray code 1111.

Binary input	Gray output
0000	0000
0001	0001
0010	0011
0011	0010
0100	0110
0101	0111
0110	0101
0111	0100
1000	1100
1001	1101
1010	1111
1011	1110
1100	1010
1101	1011
1110	1001
1111	1000

Observation

- All 16 possible 4-bit binary inputs were verified.
- The outputs match the expected Gray code values.
- The most significant bit remains unchanged.
- Only one bit changes between consecutive Gray code values.

a	b	c	d	x	y	z	u
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

Conclusion

The 4-bit Binary-to-Gray Code Converter was designed using 3 XOR gates and 1 direct connection and simulated in Logisim. All 16 input combinations were verified using the truth table. The circuit produces the correct Gray code output, ensuring that. consecutive Gray code values differ by only one bit. This demonstrates the practical application of Boolean logic in digital circuit design.

Applications & GitHub Repository

Applications:

- Rotary Encoders
- Position Sensors
- Digital Counters
- Digital Communication Systems

GitHub Repository:

Repository name: Binary-to-Gray-Code-Converter

Files included:

- **README.md** — project explanation and Boolean equations.
- **binary_to_gray.circ** — Logisim circuit file
- images/ — circuit and simulation screenshots

GitHub Repository URL: https://github.com/anjana-varma/-KLH-FED-2026-Session13-Batch-6-

Thank You

Any Question??